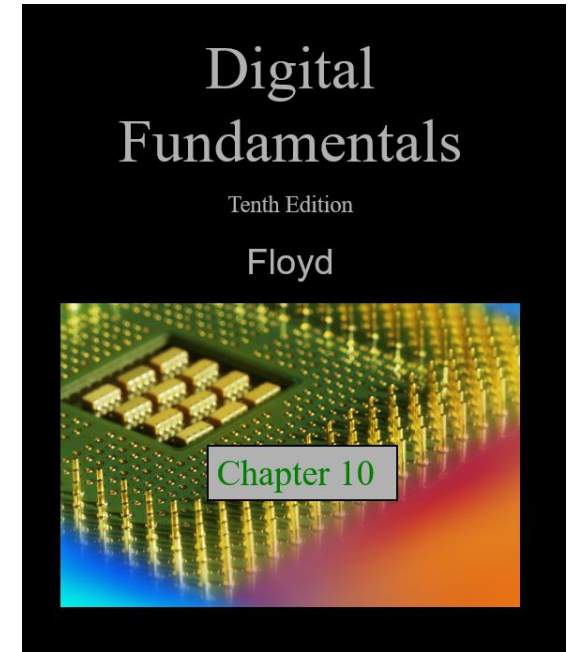


# 최신디지털공학

# Digital Fundamentals

Thomas L. Floyd



## Chapter 10

# 메모리

Memory

# Summary

## Memory Units

Memories store data in units from one to eight bits. The most common unit is the **byte**, which by definition is 8 bits.



Computer memories are organized into multiples of bytes called words. Generally, a word is defined as the number of bits handled as one entity by a computer. By this definition, a word is equal to the internal register size (usually 16, 32, or 64 bits).

For historical reasons, assembly language defines a word as exactly two bytes. In assembly language, a 32 bit entity is called a double-word and 64 bits is defined as a quad-word.

# Summary

## Memory Units

The location of a unit of data in a memory is called the **address**. In PCs, a byte is the smallest unit of data that can be accessed.

In a 2-dimensional array, a byte is accessed by supplying a row number. For example the blue byte is located in row 7.


1							
2							
3							
4							
5							
6							
7							
8							

# Summary
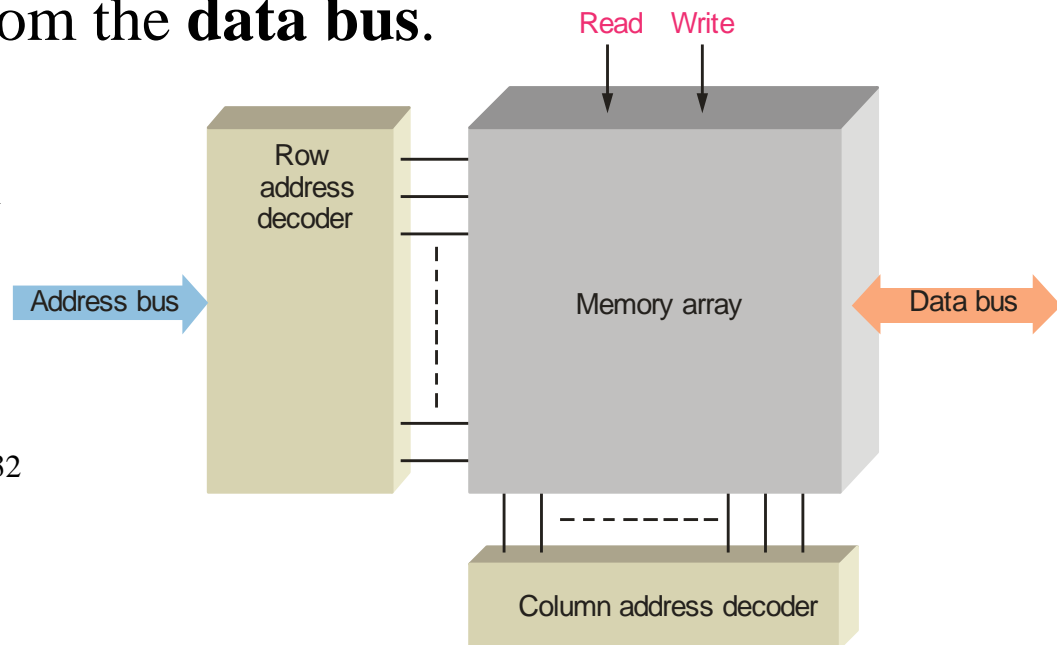
## Memory Addressing

In order to read or write to a specific memory location, a binary code is placed on the **address bus**. Internal decoders decode the address to determine the specific location. Data is then moved to or from the **data bus**.


The address bus is a group of conductors with a common function. Its size determines the number of locations that can be accessed. A 32 bit address bus can access  $2^{32}$  locations, which is approximately 4G.



# Summary
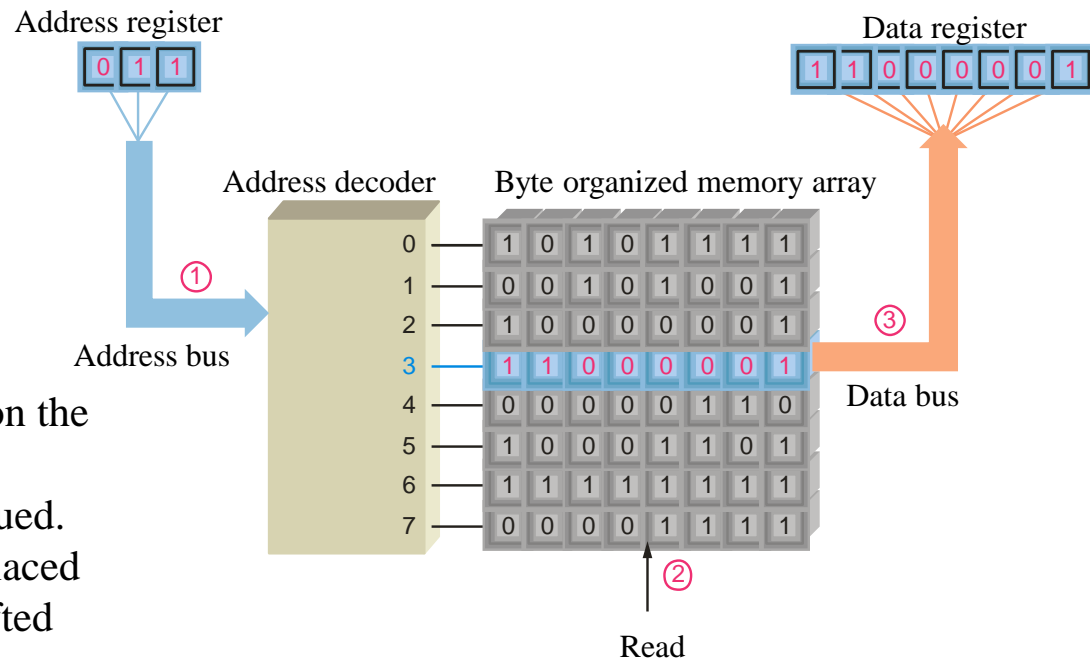
## Read and Write Operations

The read operation is actually a “copy” operation, as the original data is not changed. The data bus is a “two-way” path; data moves *from* the memory during a read operation.




1. The address is placed on the address bus.
2. A read command is issued.
3. A copy of the data is placed in the data bus and shifted into the data register.

# Summary
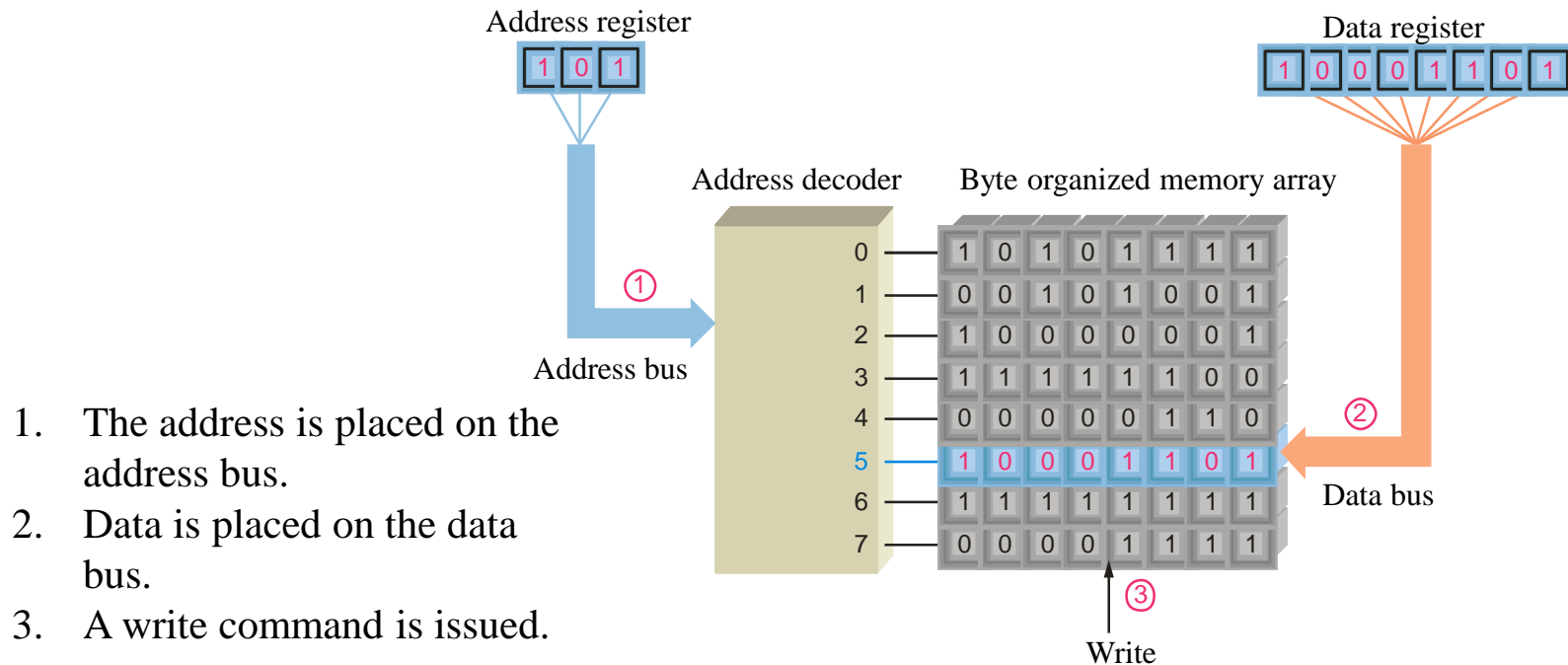
## Read and Write Operations

The two main memory operations are called **read** and **write**. A simplified write operation is shown in which new data overwrites the original data. Data moves *to* the memory.



# Summary

## RAM(Random Access Memory)

- Volatile (contents lost when the power is turned off)
- Read and write
- Large in comparison to ROM




## ROM(Read Only Memory)

- Non-volatile (contents remains when power is turned off)
- Read only
- Small in comparison to RAM




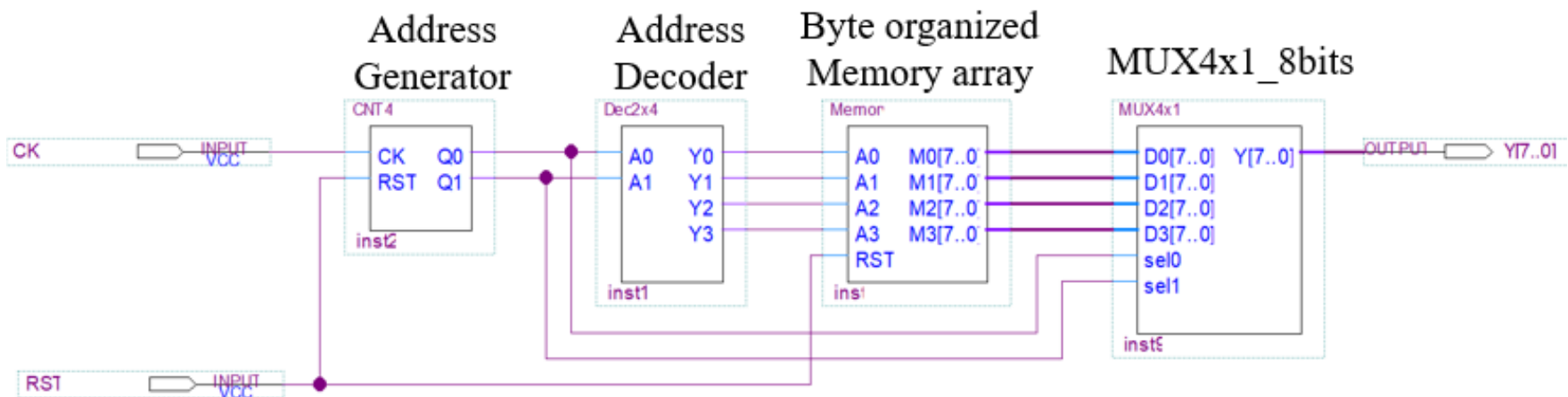
# H/W #1

아래의 Memory controller 회로를 설계하고  
그 내용을 설명하시오.





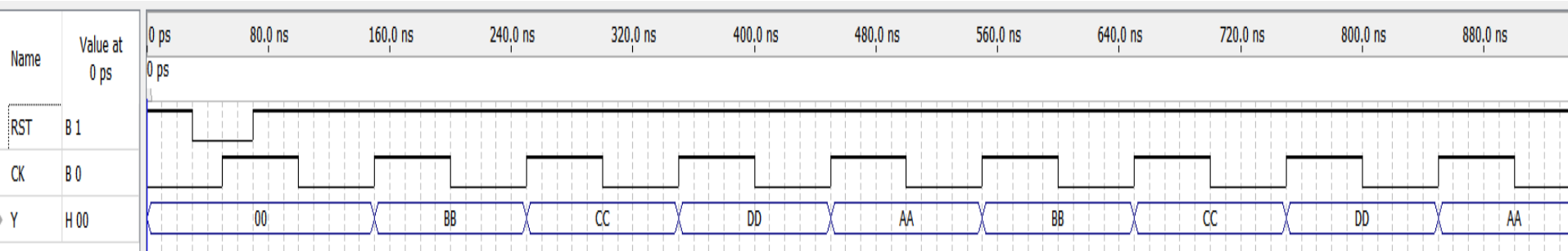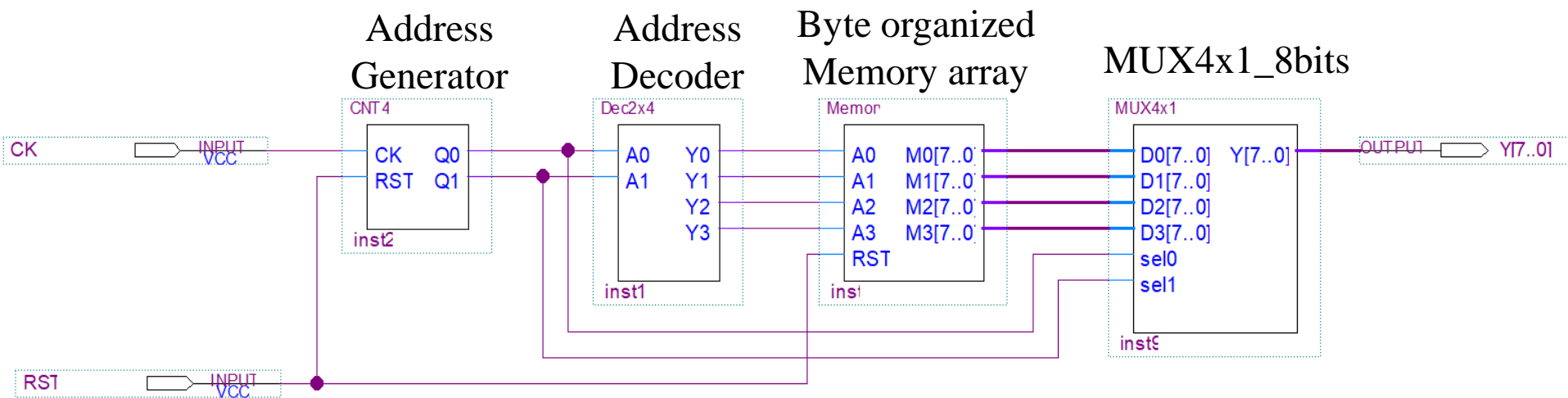

Memory 출력 data


Address 0 : AA

Address 1 : BB



Address 2 : CC

Address 3 : DD


# Address Generator

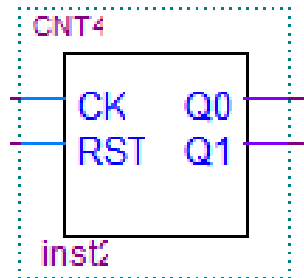


4진 Counter

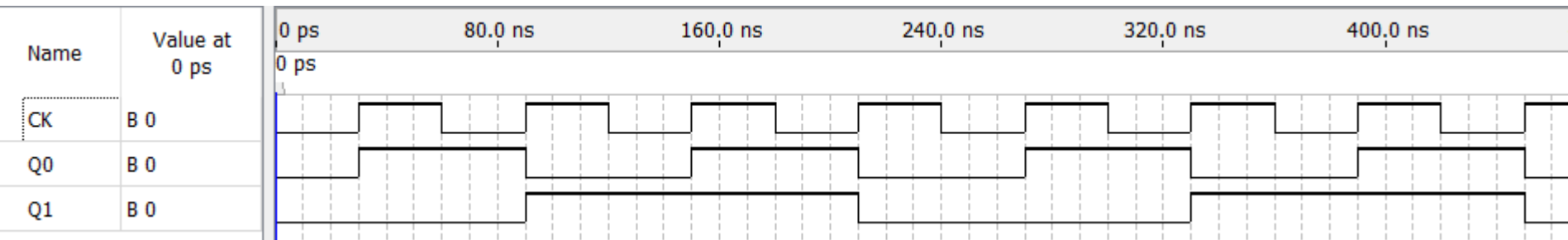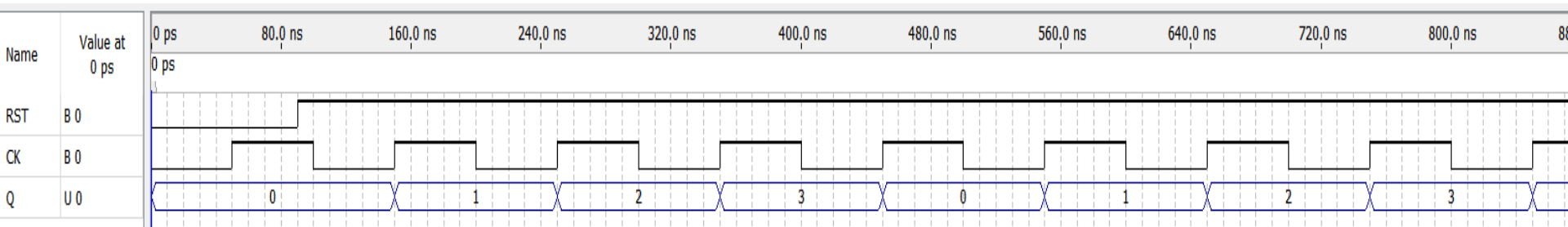

# Address Decoder

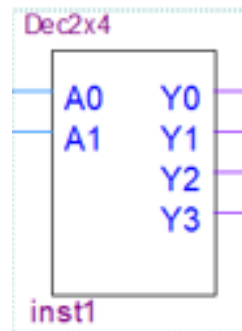


2X4 Decoder

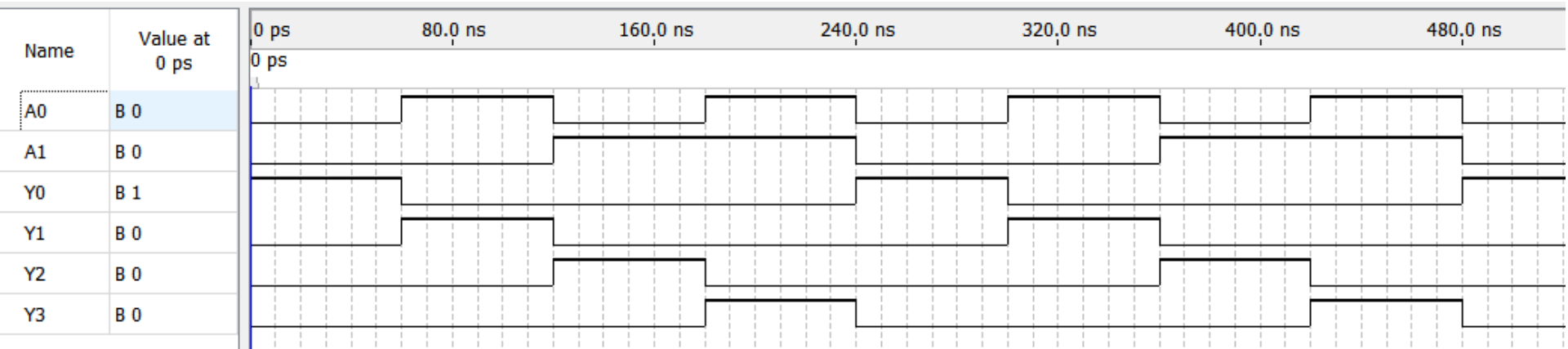

# Byte organized Memory array

4-byte Memory array

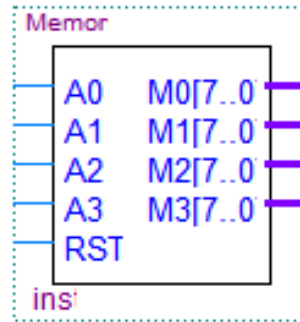



Memory 출력 data

Byte 0 : AA

Byte 1 : BB


Byte 2 : CC

Byte 3 : DD

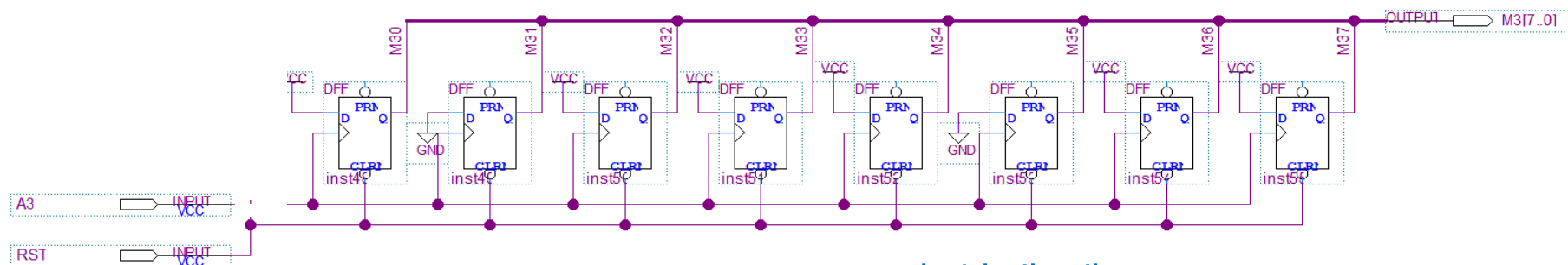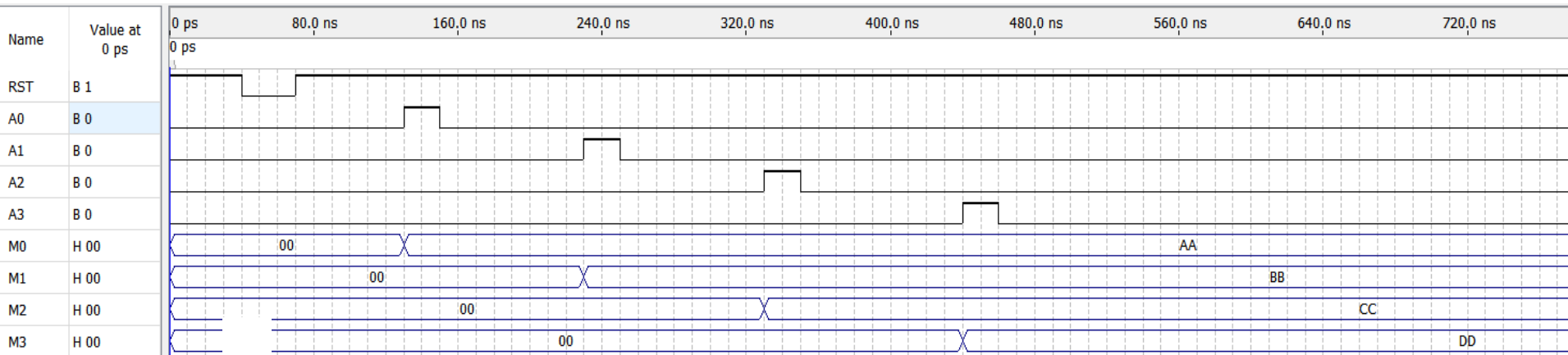

1-byte Memory array(Byte 3)의 설계 예 (DD : 11011101)
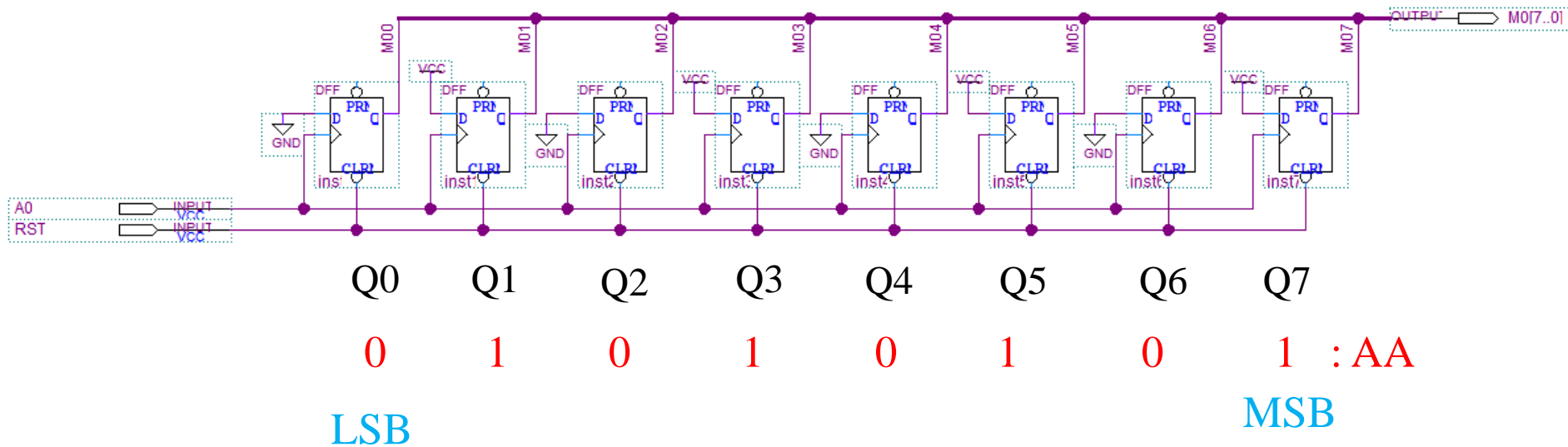
## 1-byte Memory array의 설계 예 ( AA : 10101010 )



## Quartus에서 BUS 사용법

1) 선이 굵은 BUS ICON을 눌러 드래그 하면 굵은 선의 BUS가 그려진다

Wire(bit) BUS




2) Input, Output pad에 BUS의 크기를 적는다. M0[7..0] : 8bit Bus




[7..0] 형식에 유의할 것

3) D F/F을 BUS에 wire로 연결한다.


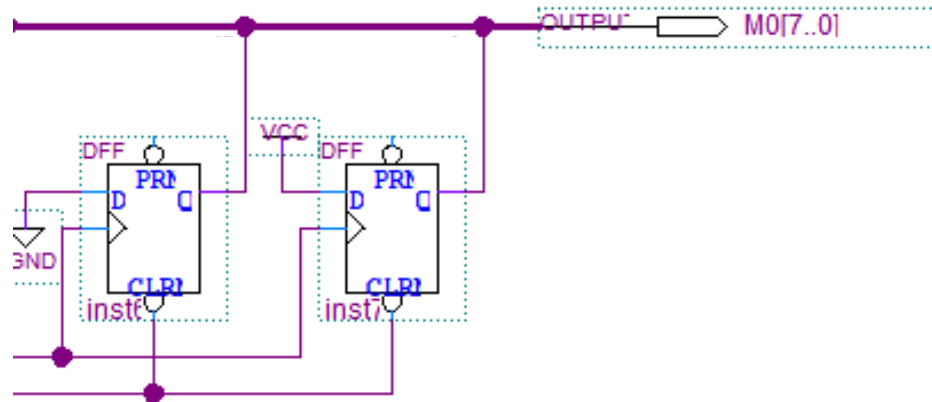


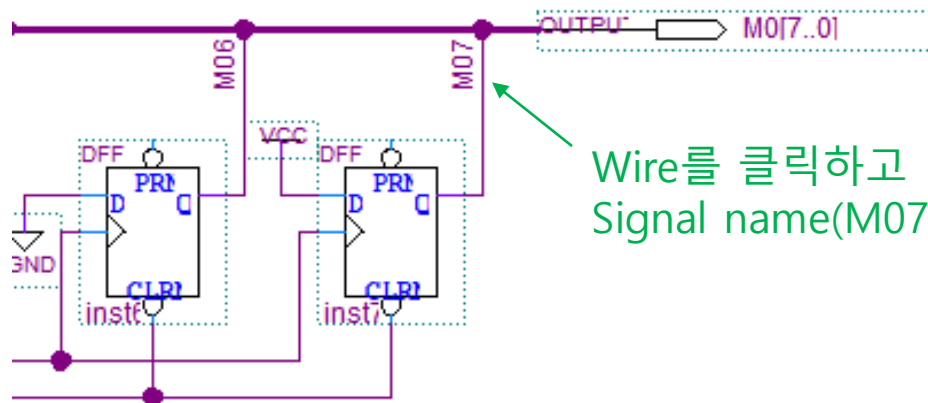4) BUS에 연결한 각각의 wire에 name을 추가한다.(M00 ~ M07)





Wire를 클릭하고  
Signal name(M07)을 타이핑 한다.


# MUX4x1\_8bits

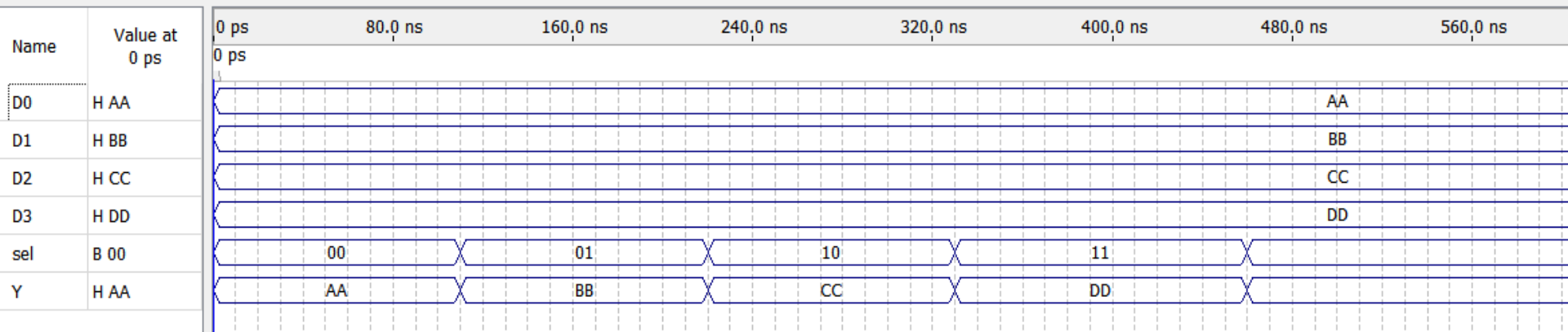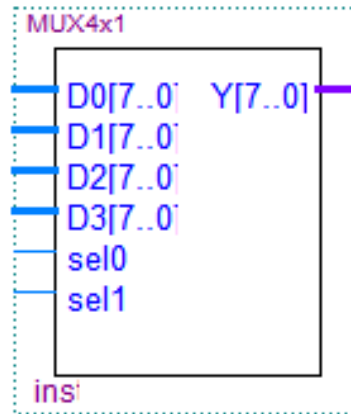


# MUX4x1\_1bit

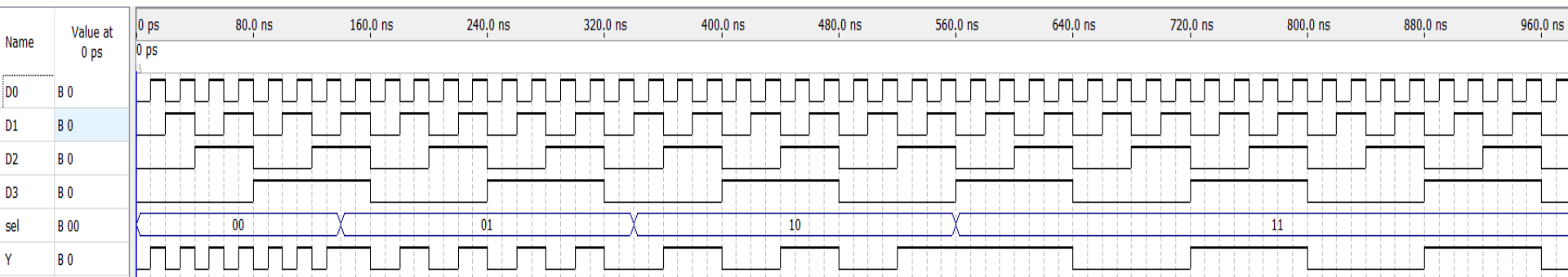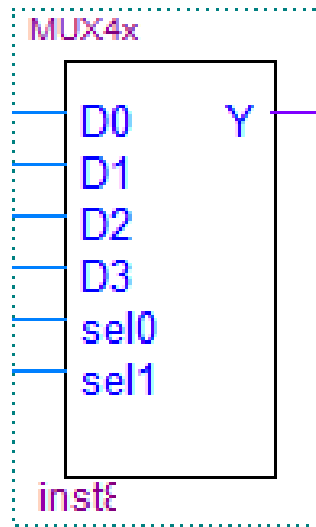



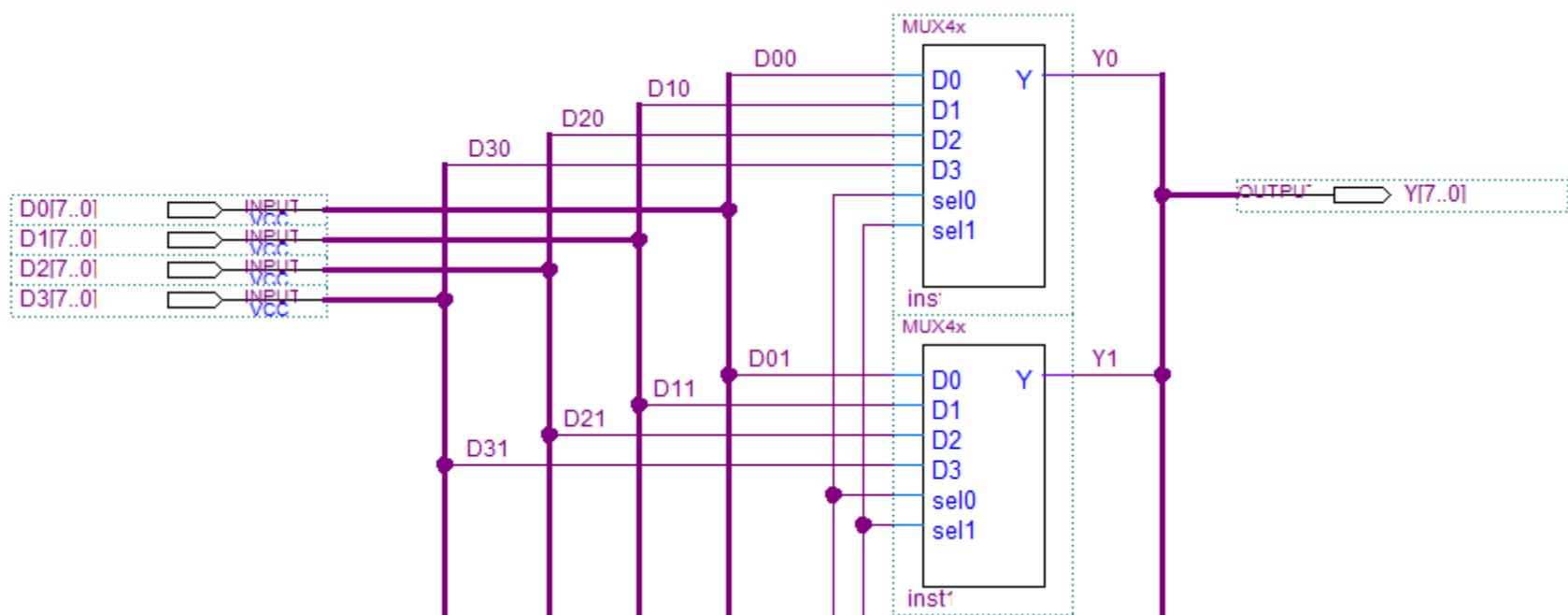

...

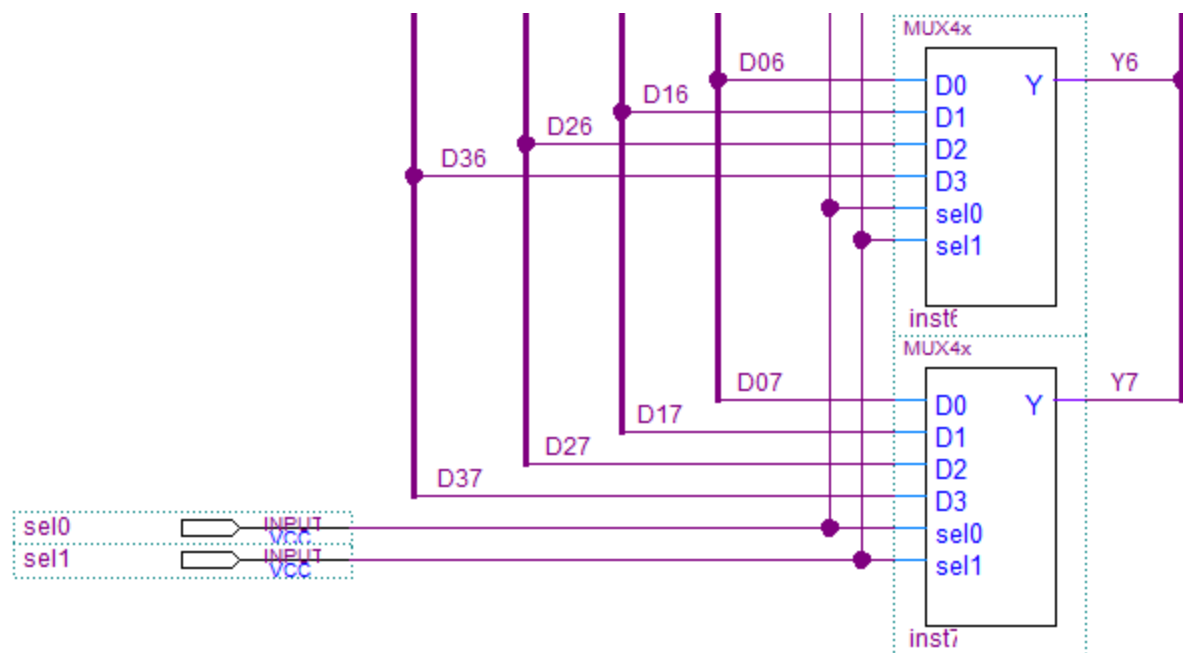








50



생산현황  
23450EA



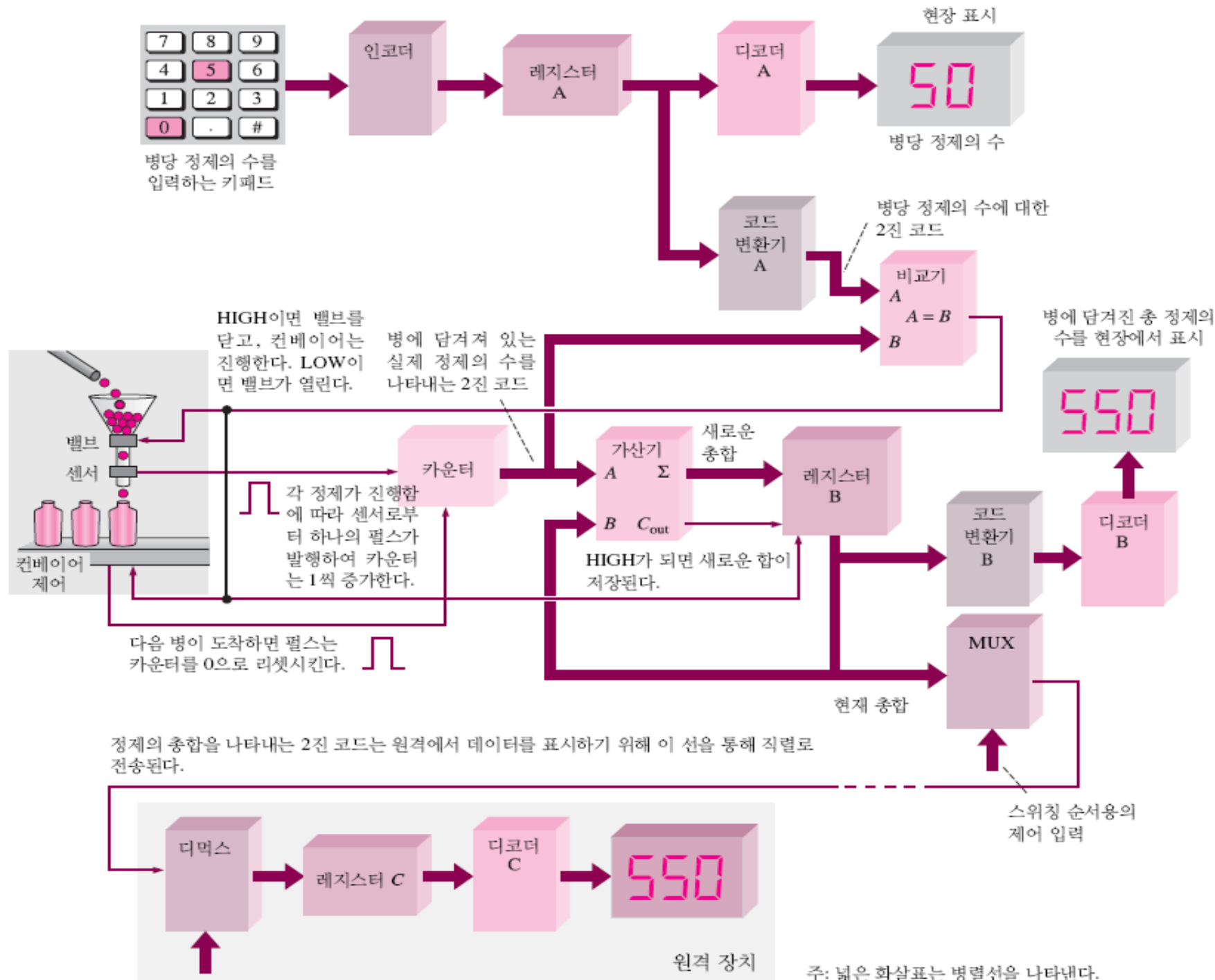



# 수고하셨습니다!!!

